

IR Remote Controlled DC Motor Circuit (Arduino Mega + L293D + IR Receiver)

1) Arduino Mega to L293D

Mega D5 -> L293D Pin 1 (Enable)

Mega D8 -> L293D Pin 2 (Input 1)

Mega D9 -> L293D Pin 7 (Input 2)

Mega 5V -> L293D Pin 16

Mega GND -> L293D Pin 4

Mega GND -> L293D Pin 5

Mega GND -> L293D Pin 12

Mega GND -> L293D Pin 13

2) DC Motor to L293D

Motor Wire 1 -> L293D Pin 3

Motor Wire 2 -> L293D Pin 6

3) 9V Battery to L293D

Battery Positive (+) -> L293D Pin 8

Battery Negative (-) -> GND rail

4) Common Ground

Battery Negative (-) -> Arduino Mega GND

5) IR Receiver to Arduino Mega

IR OUT -> Mega D2

IR VCC -> Mega 5V

IR GND -> Mega GND

Important:

Battery negative and Mega GND must be connected together.